

**Verilog HDL语言**

# **Verilog程序设计方法**


**主讲：卢 萍**

华中科技大学计算机科学与技术学院

# Module Styles

- Modules can be specified different ways
  - **Structural** – connect primitives and modules
  - **Dataflow** – use **assign** continuous assignments  
**assign** <LHS net> = <RHS expression>;
  - **Behavioral** – use **initial** and **always** blocks
- A single module can use more than one method!
- What are the differences?

# Full Adder: Structural

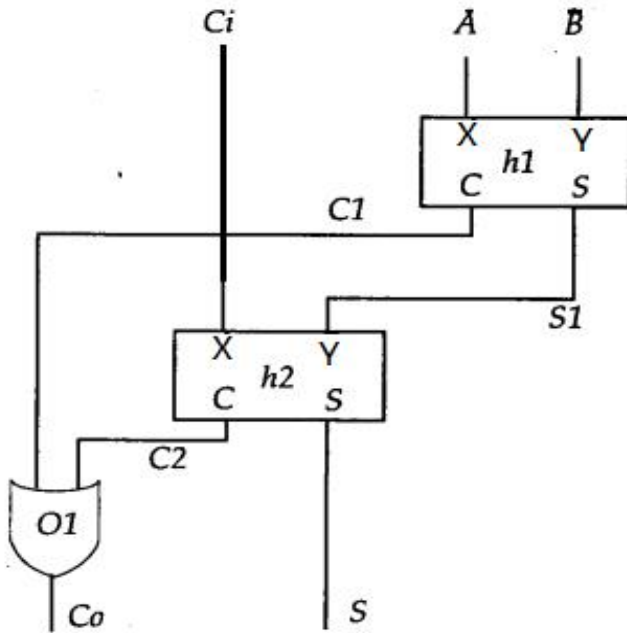

```
module half_add (X, Y, S, C);
```

```
input X, Y ;
```

```
output S, C ;
```

```
xor SUM (S, X, Y); // 异或门实例语句  
and CARRY (C, X, Y); // 与门实例语句
```

```
endmodule
```

使用两个半加器模块构造全加器

```
module full_add ( input A, B, CI, output S, CO) ;
```

```
wire S1, C1, C2;
```

```
half_add h1 (A, B, S1, C1),
```

```
           h2 (S1, CI, S, C2); //两个 半加器模块实例语句
```

```
or CARRY (CO, C2, C1); // 或门实例语句
```

```
endmodule
```

# Full Adder: Dataflow

```
module fa_rtl (A, B, CI, S, CO) ;  
  
input A, B, CI ;  
output S, CO ;  
  
// use continuous assignments  
assign S = A ^ B ^ CI;  
assign CO = (A & B) | (A & CI) | (B & CI);  
  
endmodule
```

Data flow Verilog is  
often very concise  
and still easy to read

Works great for most  
boolean and even  
datapath descriptions


# Full Adder: Behavioral

- 只要有事件发生（列表中任何 信号有变化），就执行begin...end 的语句（for simulation）  
---- 实际上，列表中信号的改变影响输出

```
module fa_bhv (A, B, CI, S, CO);  
  
input A, B, CI;  
output S, CO;  
reg S, CO;           // 只有reg型能够在 always 语句中被赋值  
  
always@(A or B or CI) // 由事件控制的always语句  
begin  
    S = A ^ B ^ CI;      // 过程性赋值语句,, 必须在 always 过程块中  
    CO = (A & B) | (A & CI) | (B & CI);  
end  
endmodule
```
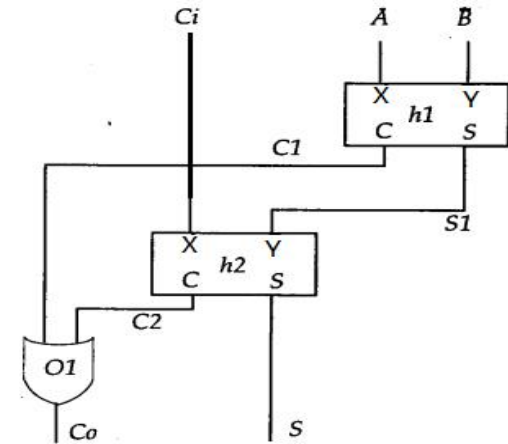
# Mix Styles

```
module Add_half_bhv(C, S, X, Y);
  output reg S, C;
  input X, Y;
  always @(X, Y) begin
    S = X ^ Y;
    C = X & Y;
  end
endmodule
```



```
module Add_full_mix(CO, S, A, B, Ci) ;
  output S, CO;
  input A, B, Ci;
  wire s1, c1, c2;
  Add_half_bhv h1(.S(s1), .C(C1), .X(A), .Y(B));
  Add_half_bhv h2(.S(S), .C(C2), .X(Ci), .Y(S1));
  assign CO = C1 | C2;
endmodule
```

# 原语(Primitives)

- 不用声明，直接实例化
- 输出端口在前，输入端口在后
- 实例名和时延可选

**and** N25(Z, A, B, C); // N25是实例名

**and** #10 (Z, A, B, X),

(X, C, D, E); // delay specified, 2 gates

**and** #10 N30 (Z, A, B); // name and delay specified

# Syntax For Structural Verilog

```
module full_add ( input A, B, CI, output S, CO );
```

```
    wire S1, C1, C2;
```

```
    half_add h1 (A, B, S1, C1), //实例化两个 half_add半加器子模块
```

```
        h2 (C1, S1, S, C2); // 端口位置关联
```

```
    or CARRY (CO, C2, C1); // 实例化或门原语
```

```
endmodule
```


```
module half_add (X, Y, S, C);
```

```
    input X, Y;
```

```
    output S, C;
```

```
    ....
```

```
endmodule
```

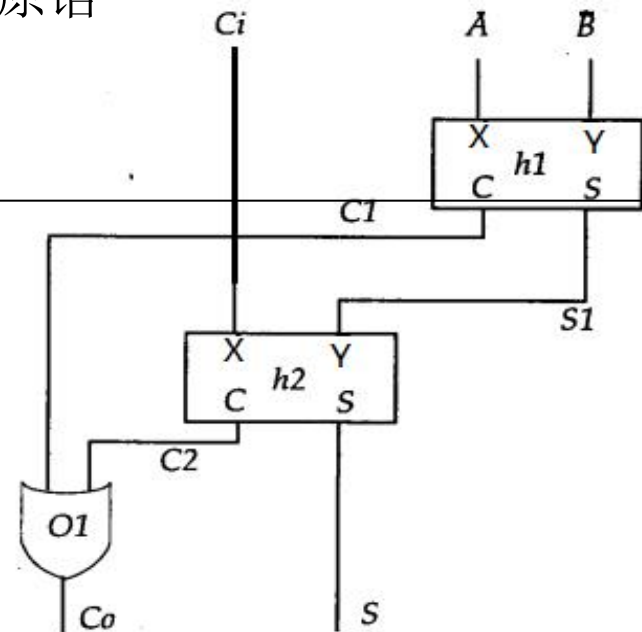



**.<port name>(<signal name>)**


```
module Add_full(Co,S, A, B, Ci) ;  
  output Co,S;  
  input A, B, Ci;  
  wire S1, C1, C2;
```

```
  Add_half h1( .C(C1), .S(S1), .X(A), .Y(B)); /* 端口名称关联 */
```

```
  Add_half h2( .C(C2), .S(S), .X(Ci), .Y(S1));
```

```
  or carry_bit(Co, C1, C2); /* 端口位置关联 */
```

```
endmodule
```

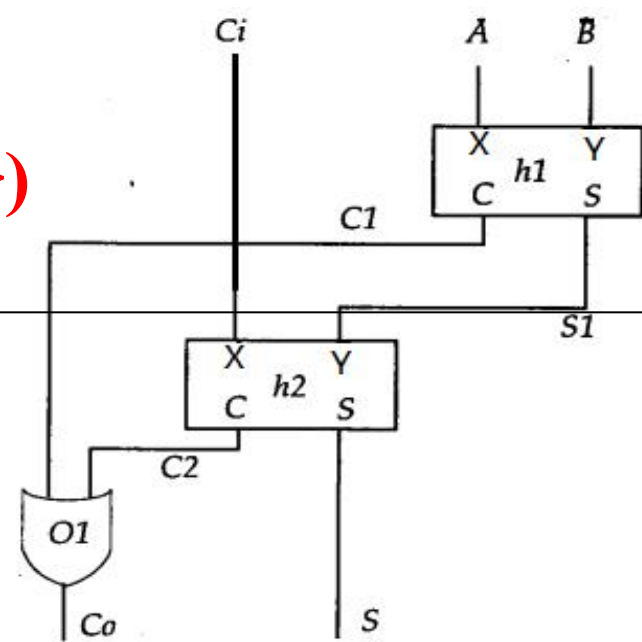

```
module half_add (X, Y, S, C);  
  input X, Y ;  
  output S, C ;  
  ....  
endmodule
```

# Empty Port Connections

- Example: **module** Add\_full(Co,S, A, B, Ci) ;
  - Add\_full AF(Cout,Sum, a, , cin) ; // B is high impedance (z)
  - Add\_full AF( ,Sum, a, b , cin) ; // Outputs Co unused.
- General rules
  - Empty input ports => high impedance state (z)
  - Empty output ports => output not used
- Specify all input ports anyway!
  - Z as an input is very bad...why?
- Helps if no connection to output port name but leave empty:
  - Add\_full AF(.Co()),.S(Sum),.A(a),.b(B) , .Ci(cin)) ;

```

module Add4bit(cout, s, a, b);
  output [3:0] s;
  output cout;
  input [3:0] a, b;
  wire cout0, cout1, cout2; // 内部信号
  Add_full A0(cout0, s[0], a[0], b[0], 1'b0);
  Add_full A1(cout1, s[1], a[1], b[1], cout0);
  Add_full A2(cout2, s[2], a[2], b[2], cout1);
  Add_full A3(cout, s[3], a[3], b[3], cout2);
endmodule

```


Example:  
Detecting cout2

Must output  
cout2


```

module Add_full (Co,S, A, B, Ci);
  input A, B, Ci ;
  output S, Co ;
  ....
endmodule

```

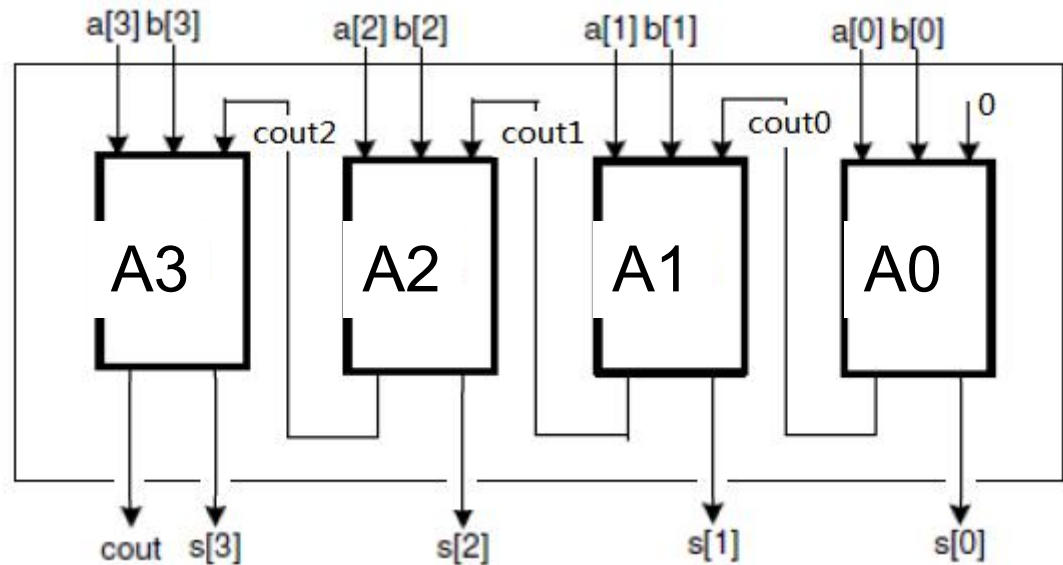



# 层次结构

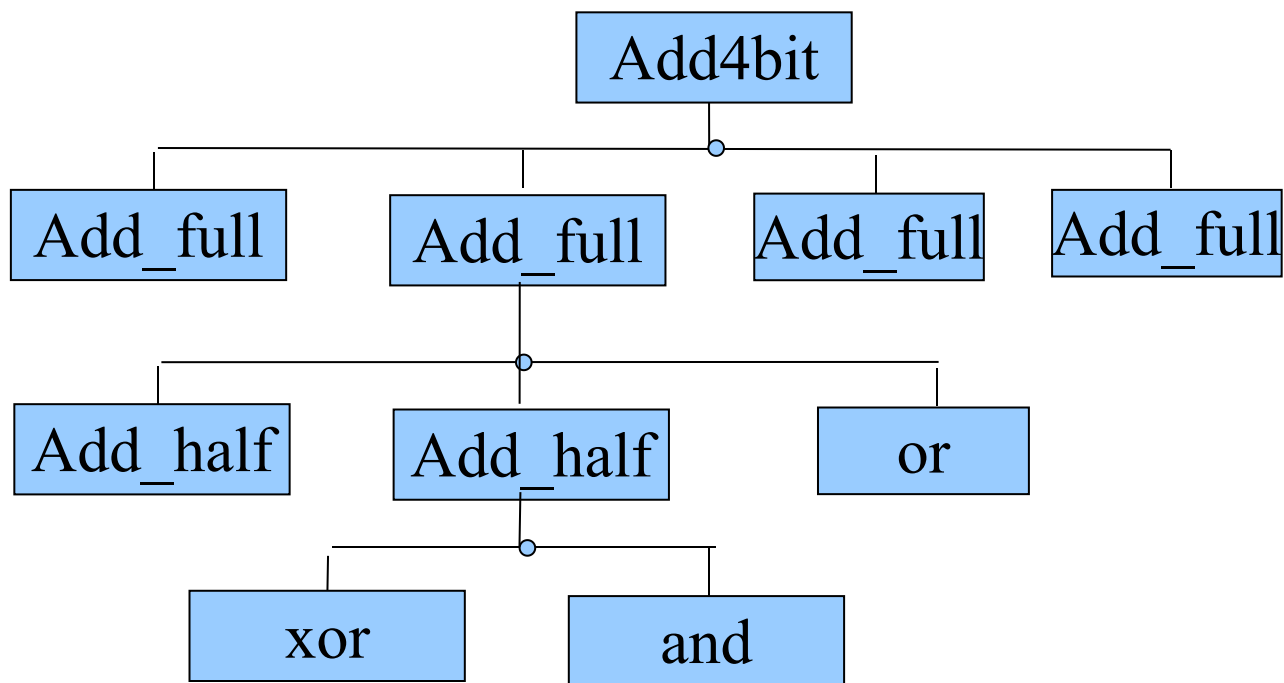

4位加法器的层次结构
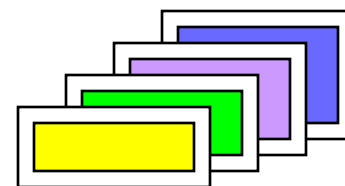 
# 层次化 与 源文件

- 多个module是放在同一个文件还是分开放?
- 可以放在同一个文件中
  - 模块次序自由
  - 适合于小设计
  - 不太适合模块重用（剪切和粘贴）
- 可以将模块分解成多个文件
  - 良好习惯：每个文件只包含一个module
  - 有助于组织模块
  - 便于找到一个模块
  - 有利于模块重用（将文件添加到项目中）




# Dataflow Verilog

- The continuous assign statement
  - It is the main construct of Dataflow Verilog
  - It is **deceptively** powerful & useful
- More basic generic form:  

```
assign [delay] <LHS_net> = <RHS_expression>;
```
- If RHS (right hand side) result changes, LHS is updated with new value
  - Constantly operating (“continuous”)
  - It's *hardware!*

# Back to the Continuous Assign

- RHS can use operators (i.e.  $+$ ,  $-$ ,  $\&$ ,  $|$ ,  $^$ ,  $\sim$ ,  $>>$ , ...)

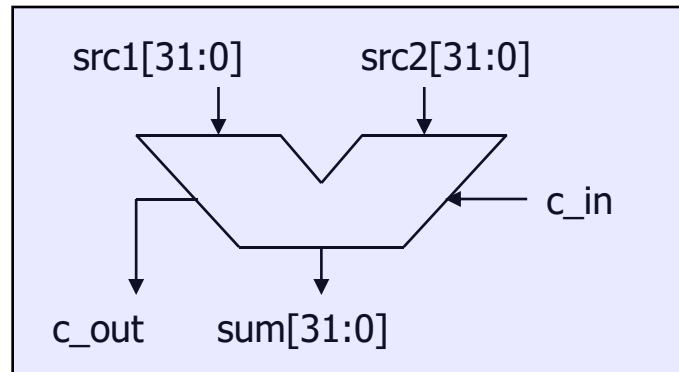

```
wire [31:0] sum, src1, src2;
```

```
wire c_in, c_out;
```

```
assign {c_out, sum} = src1 + src2 + c_in;
```

## □ Verilog运算符（9类）

- 算术运算符：+、-、\*、/、%
- 位运算符：~、&、|、^、 $\wedge\sim$  或  $\sim\wedge$ （异或非）
- 缩位运算符（单目）：&、~&(与非)、|、~|、^、 $\wedge\sim$ 、 $\sim\wedge$
- 逻辑运算符：!、&&、||
- 关系运算符（双目）：<、>、<=、>=
- 相等与全等运算符： $\mathbf{==}$ （逻辑相等）、 $\mathbf{!=}$ （逻辑不等）、 $\mathbf{===}$ （全等）、 $\mathbf{!==}$ （非全等）
- 逻辑移位运算符：<<、>>
- 连接运算符：{ }
- 条件运算符：?:



# Behavioral Verilog

- 行为建模的主要机制: **initial** and **always**
  - 所有其他的行为语句包含在这两个语句中
  - **initial** and **always** 块不能嵌套
  - 左边变量必须是 **reg** 类型
- **initial** 语句从0时刻开始执行且只执行一次
  - 如果有多个**initial**块, 它们都从0时刻开始并行独立执行, 独立完成执行.
- 如果在**initial**语句中有多条行为语句, 那么需用 **begin/end** 组合在一起。

# More on **initial** statements

- Initial statement very useful for testbenches
- Initial statements **don't** synthesize
- Don't use them in DUT (DUT: device under test)  
Verilog (stuff you intend to synthesize)

# initial Blocks

```
`timescale 1 ns / 100 fs
module full_adder_tb;
  reg [2:0] stim;
  wire s, c;

  add_full DUT (e, s, stim[2], stim[1], stim[0]); // instantiate DUT

  // monitor statement is special - only needs to be made once,
  initial $monitor("%t: s=%b c=%b stim=%b", $time, s, c, stim[2:0]);


  // tell our simulation when to stop
  initial #50 $stop;

  initial begin // stimulus generation
    for (stim = 3'h0; stim < 3'h8; stim = stim + 1) begin
      #5;
    end
  end
end
endmodule
```

*all initial blocks start at time 0*

*multi-statement block enclosed by **begin** and **end***

# Another **initial** Statement Example

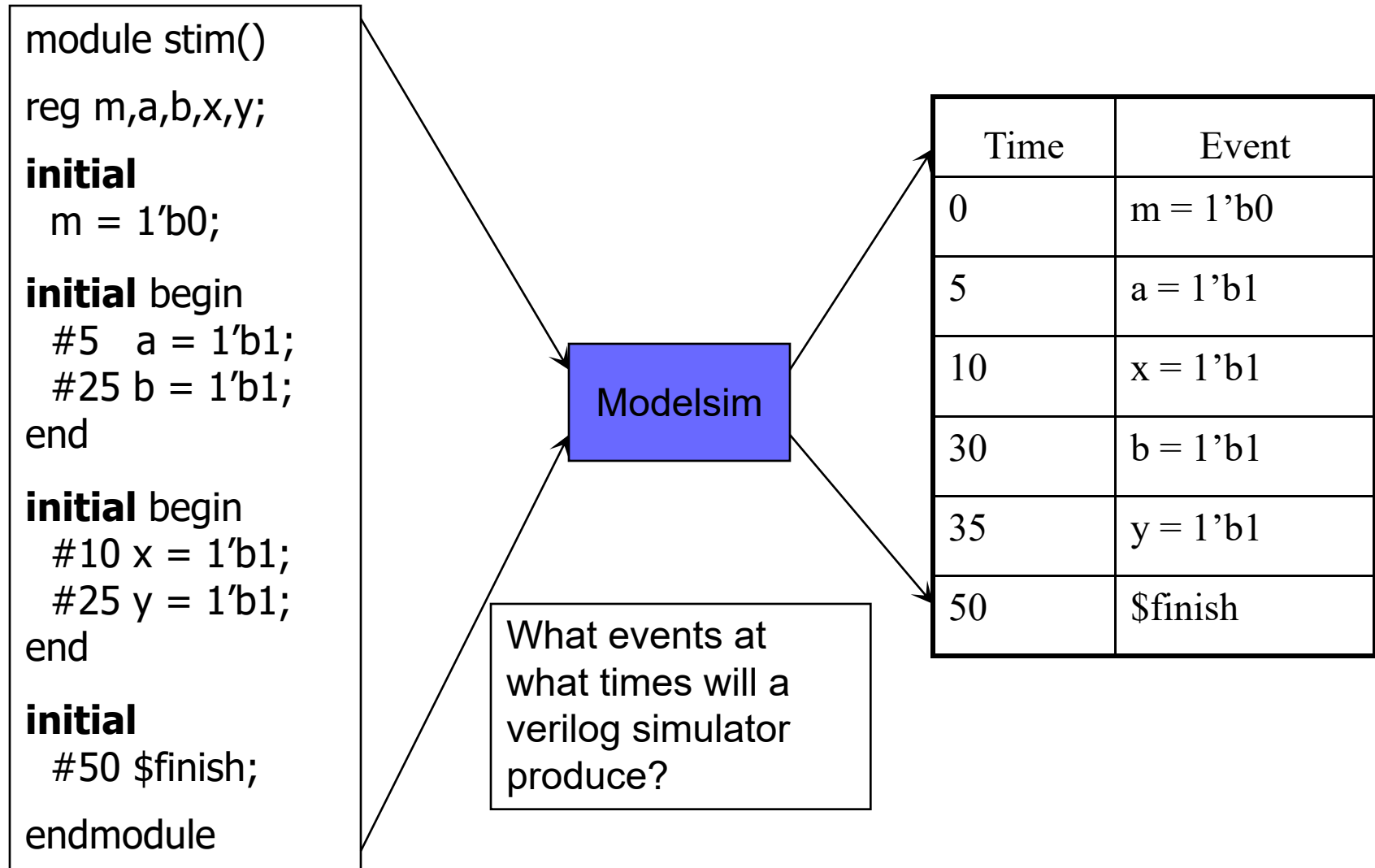

# always statements

- **always**语句重复执行
  - 从0时刻开始不断循环执行;
  - 可以使用触发/敏感事件列表来控制操作; **@(a or b or c)**
  - 没有触发事件, 将在0时刻无限循环执行。

```
module clock_gen (output reg clock);  
  
  initial  
    clock = 1'b0;           // must initialize in initial block  
  
  always          // no trigger list for this always  
    #10 clock = ~clock;    // 带有时序控制  
                           //产生周期为20时间单位的波形  
  
endmodule
```

# always的事件控制方式

- **always**是基于事件执行，有两种类型的事件控制方式
  - 边沿触发事件控制:用来描述时序逻辑电路
  - 电平敏感事件控制:用来描述组合逻辑电路
- **always @(posedge clk)** // clk从低电平->高（正沿）  
    cur\_state=next\_state; // 就执行赋值语句
- **always @(negedge reset)** // reset从高->低（负沿）  
    count=0; // 就执行赋值语句
- **always @ (posedge clear or negedge reset)**  
    Q=0;
- 不可以同时包括同一个信号的上升沿和下降沿

# 电平敏感信号列表

- 只要列表内有信号发生电平变化，就执行该 **always** 结构中的内容。
- Original way to specify trigger list  
**always @ (X1 or X2 or X3)**
- In Verilog 2001 can use , instead of **or**  
**always @ (X1, X2, X3)**
- Verilog 2001 also has \* for *combinational only*  
**always @ (\*)** //“\*”代表所有输入信号，可防止遗漏
- 不可以同时包括电平敏感事件和边沿敏感事件

Some mixed simulation tools in use today still do not support Verilog 2001.

# Example: 比较器

```
module compare_4bit_behave(output reg A_gt_B, A_lt_B, A_eq_B,  
                           input [3:0] A, B);
```

```
  always@( A or B) begin
```

```
    if ( A > B )
```

```
        { A_gt_B, A_lt_B, A_eq_B } = 3'b100;
```

```
    else if ( A == B)
```


```
        { A_gt_B, A_lt_B, A_eq_B } = 3'b001;
```

```
    else
```

```
        { A_gt_B, A_lt_B, A_eq_B } = 3'b010;
```

```
  end
```

```
endmodule
```

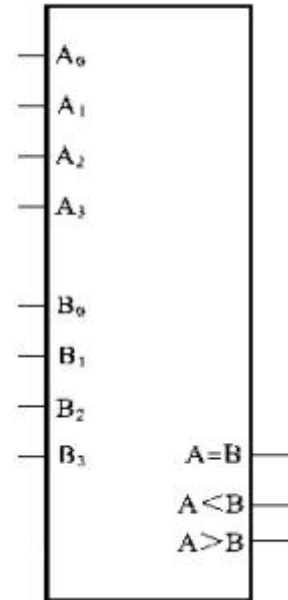

Flush out this template with sensitivity list and implementation  
**Hint:** a if...else if...else statement is best for implementation



## □ if-else 条件语句

```
if (条件表达式)      块语句1  
else if (条件表达式2) 块语句2  
.....  
else if (条件表达式n) 块语句n  
else                  块语句n+1
```

## □ case 语句

```
case (敏感表达式)  
  值1:      块语句1  
  值2:      块语句2  
  .....  
  值n:      块语句n  
  default:  块语句n+1  
endcase
```

## □ for循环语句

```
for (表达式1; 表达式2; 表达式3) 块语句
```

# if...else if...else statement

- General forms...

```
If (condition) begin  
    <statement1>;  
    <statement2>;  
end
```


Of course the compound statements formed with **begin/end** are optional.

```
If (condition)  
begin  
    <statement1>;  
    <statement2>;  
end  
else  
begin  
    <statement3>;  
    <statement4>;  
end
```

```
If (condition)  
begin  
    <statement1>;  
    <statement2>;  
end  
else if (condition2)  
begin  
    <statement3>;  
    <statement4>;  
end  
else  
begin  
    <statement5>;  
    <statement6>;  
end
```
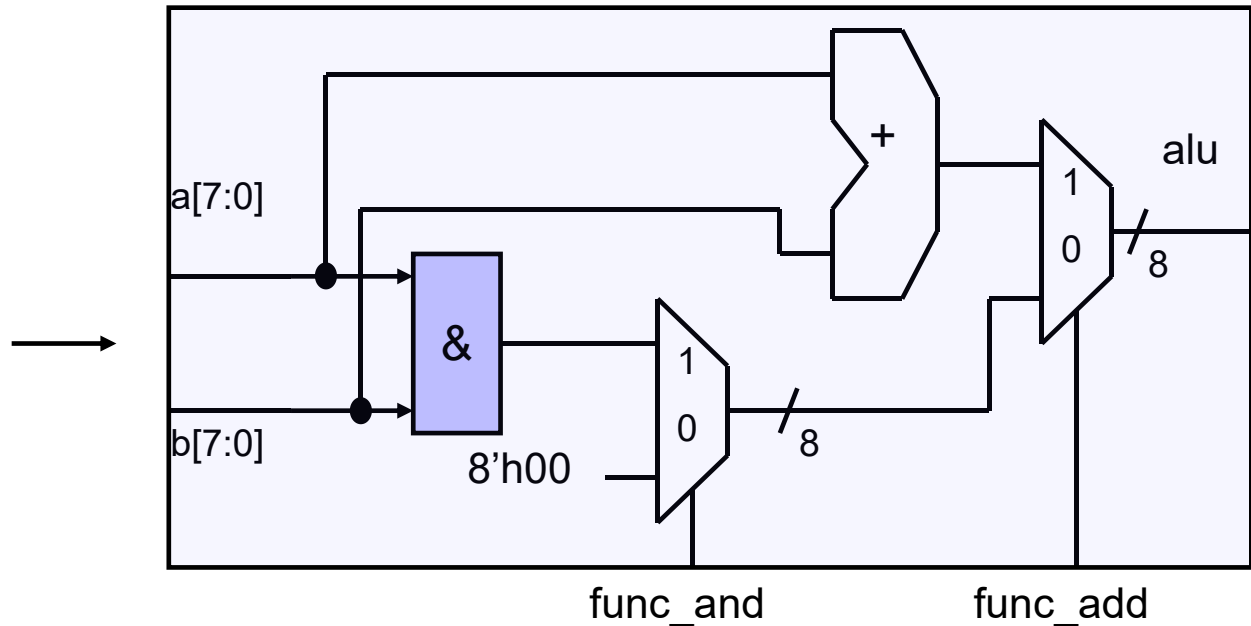
# How does and if...else if...else statement synthesize?

```
if (func_add)
    alu = a + b;
else if (func_and)
    alu = a & b;
else
    alu = 8'h00;
```




# if statement synthesis (continued)

```
if (a)  
  func = c & d;  
else if (b)  
  func = c | d;
```

How does this  
synthesize?

if 要加上else，以防  
止锁存器的发生

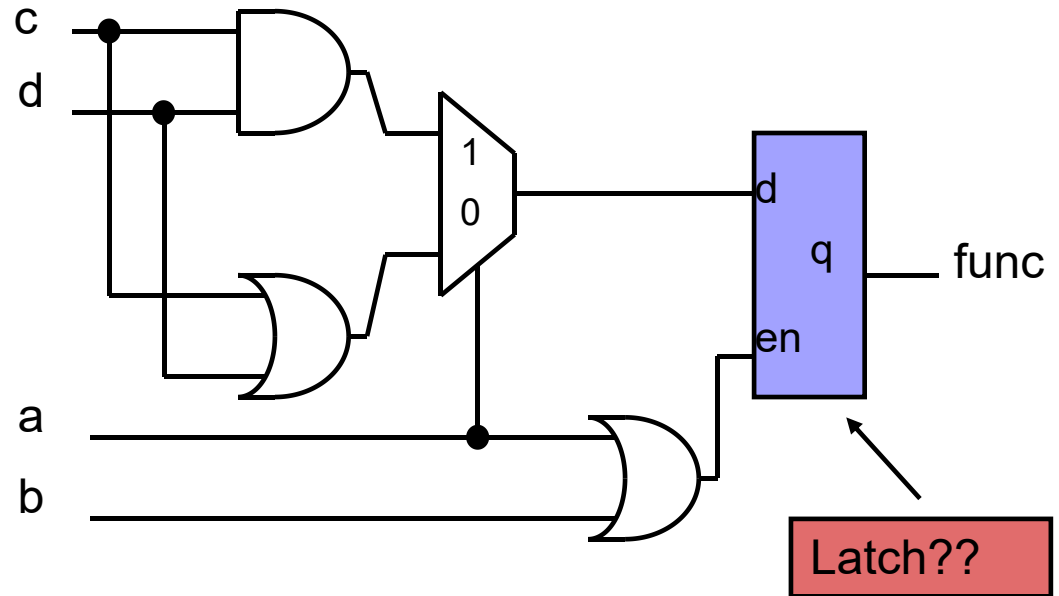

语句不完整即有某些情况的输入对输出无任何影响，根据锁存器的特征，反映到硬件电路即会产生锁存器。

# More on **if** statements...

- Watch the sensitivity lists...what is missing in this example?

```
always @(a, b) begin  
    temp = a - b;  
    if ((temp < 8'b0) && abs)  
        out = -temp;  
    else out = temp;  
end
```

注意敏感信号的完备性：  
必须将所有的输入信号和  
条件判断信号都列在信号  
列表中。

//带同步清0、同步置1的D触发器

```
always @ (posedge clk) begin  
    if (reset) q <= 0;  
    else if (set) q <= 1;  
    else q <= data;  
end
```

What is being coded here?

Is it synchronous or asynch?

Does the reset or the set have  
higher priority?

# Example: 7段数码管的显示译码器

```
module _7seg_display( in,SEG);
    input [3:0] in;    // 二进制输入
    output reg[7:0] SEG; // 7-seg display 输出。0--ON, 1--OFF
                        // 对应关系, SEG[0]->a,SEG[1]->b, ...
```

```
always@( in ) begin
```

```
    case (in[3:0])
```

```
        4'b0000 : SEG = 8'b11000000; // 0
        4'b0001 : SEG = 8'b11111001; // 1
        4'b0010 : SEG = 8'b10100100; // 2
        4'b0011 : SEG = 8'b10110000; // 3
        4'b0100 : SEG = 8'b10011001; // 4
        4'b0101 : SEG = 8'b10010010; // 5
        4'b0110 : SEG = 8'b10000010; // 6
        4'b0111 : SEG = 8'b11111000; // 7
        4'b1000 : SEG = 8'b10000000; // 8
        4'b1001 : SEG = 8'b10010000; // 9
        4'b1010 : SEG = 8'b10000110; // E
        default : SEG = 8'b11111111; // All OFF
```


```
    endcase
```

```
end
```

```
endmodule
```

h g f e d c b a

显示0: 1 1 0 0 0 0 0 0

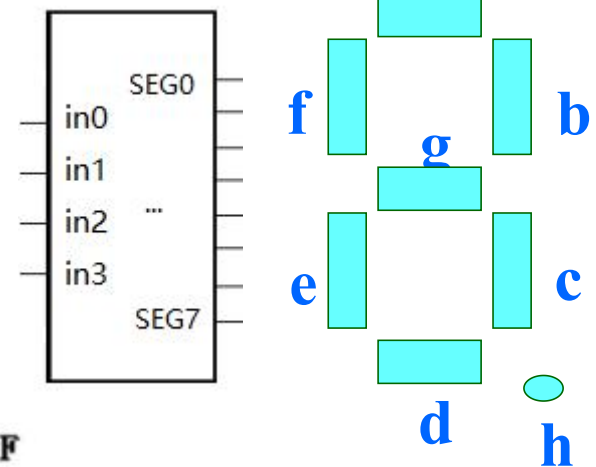

# case Statements

---

- Verilog 有3种形式的case语句:
  - ⑩ **case**, **casex**, and **casez**
- 表达式按顺序与各分支项值按位匹配
  - 两者位宽相同!
- **case**: 是一种全等比较
  - Can detect **x** and **z** ! (good for testbenches)
- **casez**
  - 比较双方有一方的某些位的值是**z**, 那么这些位的比较就**不予考虑**, 而只关注其他位的比较结果
- **casex**
  - 比较双方有一方的某些位的值是**x**和**z**, 就**不予考虑**
- ? 可用来代替**z**, 表示无关位

```


if (func_add)
    alu = a + b;
else if (func_and)
    alu = a & b;
else alu = 8'h00;

```

```

case({func_add, func_and})
    2'b00: alu = 8'h00;
    2'b01: alu = a & b;
    2'b1x: alu = a + b;
    default: alu = 8'h00;
endcase

```

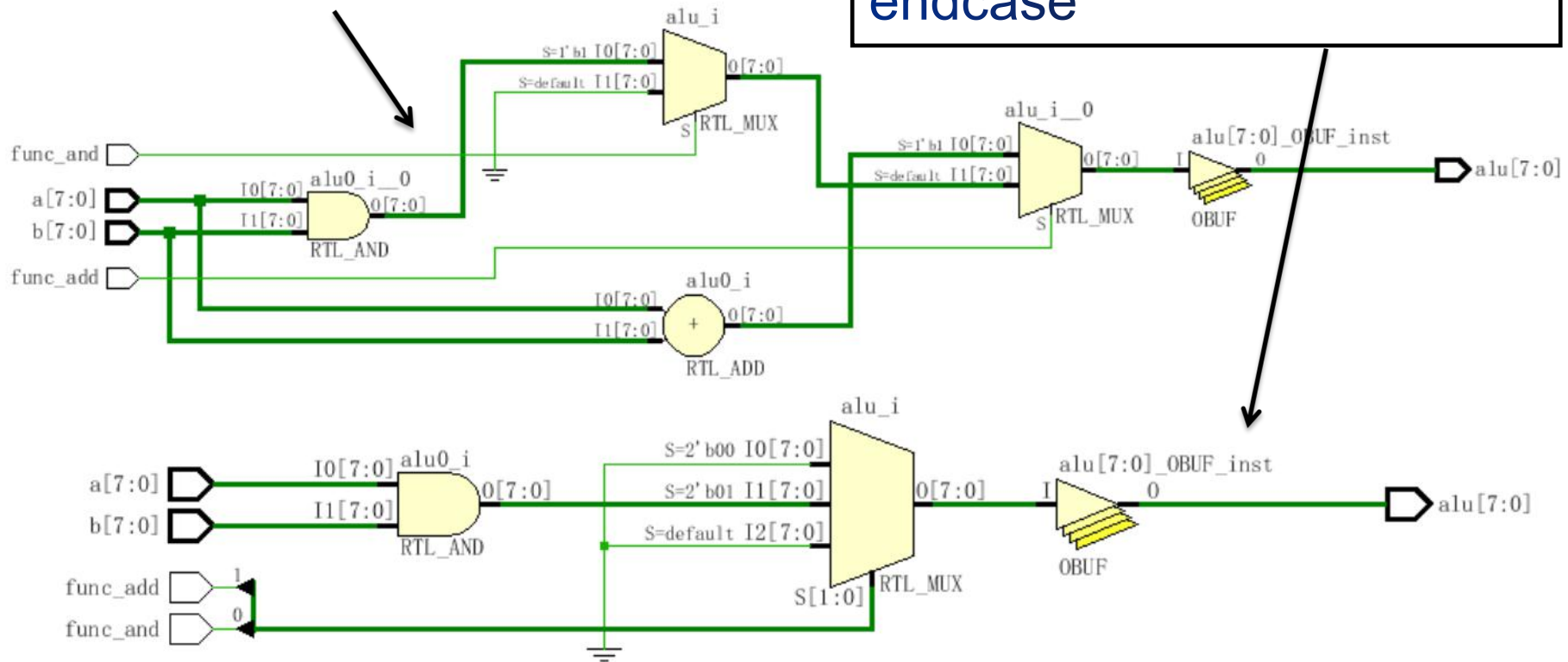

case的index列表里的x和z，都被综合工具认为是不可达状态,被去掉了。



# Loops in Verilog

---

- We already saw the **for** loop:

```
reg [15:0] rf[0:15]; // memory structure for modeling register file
reg [5:0] w_addr;    // address to write to

for (w_addr=0; w_addr<16; w_addr=w_addr+1)
    rf[w_addr[3:0]] = 16'h0000;    // initialize register file memory
```

- There are 3 other loops available:
  - While loops
  - Repeat loop
  - Forever loop

# while loops

---

- Executes until boolean condition is not true

⑩ If boolean expression false from beginning it will never execute loop

```
reg [15:0] flag;  
reg [4:0] index;  
  
initial begin // 找非0标志位  
    index=0;  
    found=1'b0;  
    while ((index<16) && (!found)) begin  
        if (flag[index]) found = 1'b1;  
        else index = index + 1;  
    end  
    if (!found) $display("non-zero flag bit not found!");  
    else $display("non-zero flag bit found in position %d",index);  
end
```

Handy for cases where  
loop termination is a more  
complex function.

Like a search

# repeat Loop

- 执行指定的循环次数
  - ⑩ Repeat的循环次数可以是一个变量，但
    - ✓ 其值在开始循环时得到计算，从而得以事先确定循环次数
    - ✓ 如果其值在循环执行期间发生更改，也不会更改迭代次数
- 在testbench，常与 @(posedge clk) 事件控制一起使用，用来等待固定数量的时钟。

```
initial begin
```

```
inc_DAC = 1'b1;           // 等待clk的4095个正沿
repeat(4095) @(posedge clk); // bring DAC right up to point of rollover
inc_DAC = 1'b0;
inc_smpl = 1'b1;
repeat(7)@(posedge clk);    // bring sample count up to 7
inc_smpl = 1'b0;
```

```
end
```

# forever loops

---

- 无限循环。常用于产生周期性的波形，用来作为仿真测试信号。它与**always**的不同之处是不能独立在程序中，**必须写在initial块中**
- Only a **\$stop**, **\$finish** or a specific **disable** can end a **forever** loop.

```
initial begin
    clk = 0;
    forever    //每隔10个时间单位clk反相一次
        #10 clk = ~ clk;
end
```

Clock generator is by far the most common use of a forever loop

```
module mult4b(output reg [7:0] R, input [3:0] A, input [3:0] B);
```

```

A:      1101
B:      1011
* -----
          1101
         1101
        1101
       +-----
      10001111

```



# 过程赋值语句

## ❑ 阻塞型过程赋值：=

前一条语句没有完成赋值过程之前，后面的语句不能被执行

## ❑ 非阻塞型过程赋值：<=

一条非阻塞赋值语句的执行，不会影响块中其它语句的执行

**基本形式：** <寄存器变量>=<表达式>;

**外部模式：** <定时控制> <寄存器变量>=<表达式>; //定时满足，RHS被计算和赋值

**内部模式：** <寄存器变量>= <定时控制> <表达式>; //计算RHS，定时满足后再赋值


**定时控制分为两类：** 延时控制 #delay

事件控制 @(事件控制敏感表)
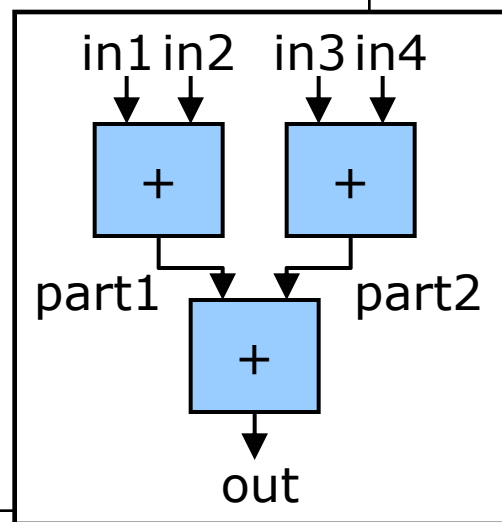
# 阻塞性赋值

- 当前的赋值语句阻断了其后的语句，即后面的语句必须等到当前的赋值语句执行完毕才能执行
- Works a lot like software (**danger!**)
- 用于组合逻辑


```
module addtree(output reg [9:0] out,  
               input [7:0] in1, in2, in3, in4);  
  
  reg [8:0] part1, part2;  
  always @(in1, in2, in3, in4) begin  
    part1 = in1 + in2;  
    part2 = in3 + in4;  
    out = part1 + part2;  
  
  end  
endmodule
```


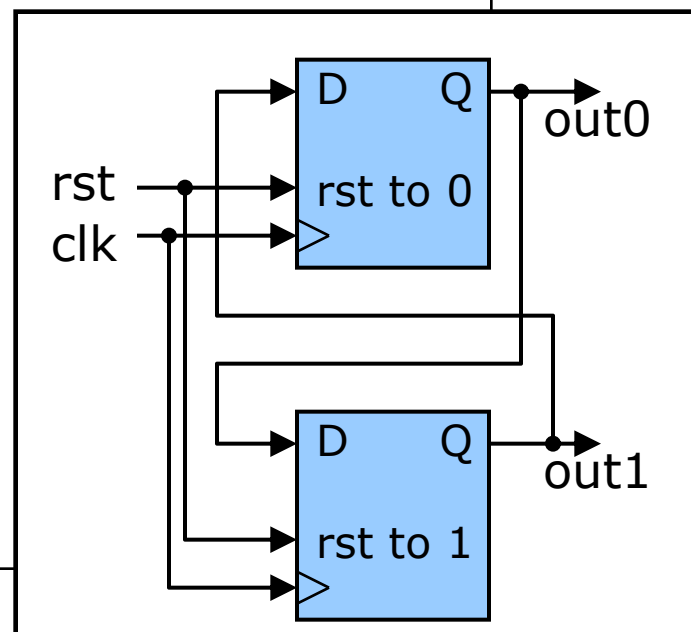
# 非阻塞性赋值

- 如果没有定时控制，则同时计算RHS和更新LHS
- 用于时序逻辑
- 只能用在"initial"和"always"中

```
module swap(output reg out0, out1, input rst, clk);  
  always @(posedge clk) begin  
    if (rst) begin  
      out0 <= 1'b0;  
      out1 <= 1'b1;  
    end  
    else begin  
      out0 <= out1;  
      out1 <= out0;  
    end  
  end  
endmodule
```





# Swapping if done in Blocking

- In blocking, need a “temp” variable

```
module swap(output reg out0, out1, input in0, in1, swap);
```

```
reg temp;
```

```
always @(*) begin
```

```
    out0 = in0;
```

```
    out1 = in1;
```

```
    if (swap) begin
```

```
        temp = out0;
```


```
        out0 = out1;
```

```
        out1 = temp;
```

```
    end
```

```
end
```


```
endmodule
```

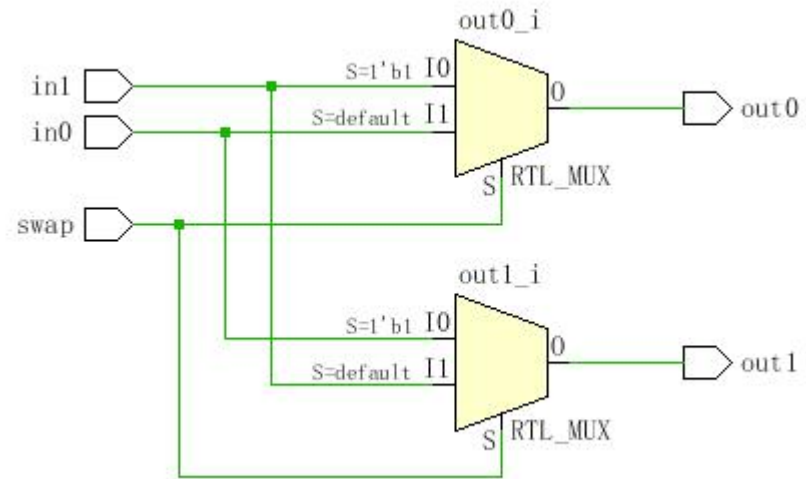

**Which values get included on the sensitivity list from \*?**
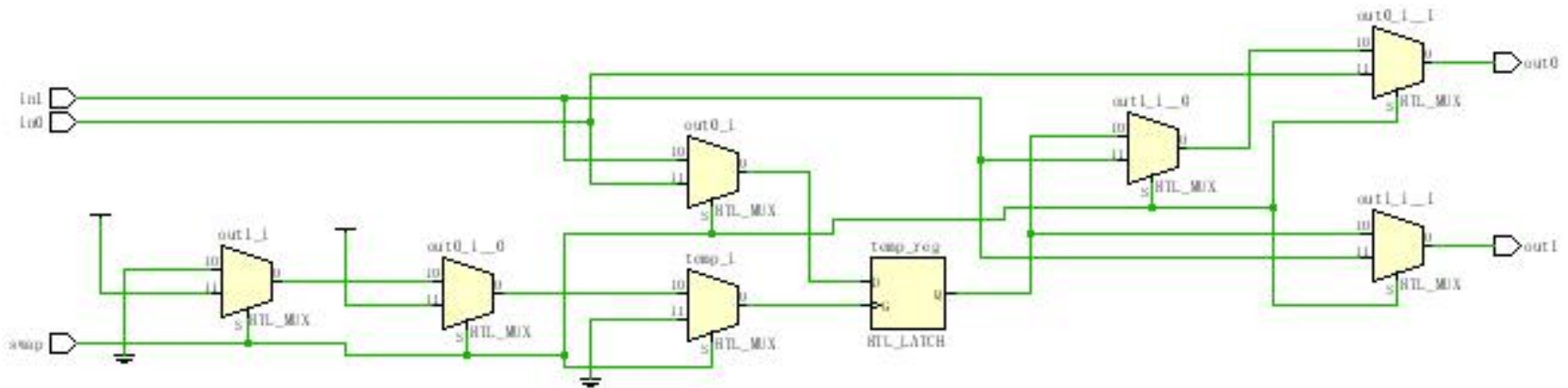
# Swapping if done in Non-Blocking


```
module swap(output reg out0, out1, input in0, in1, swap);  
  reg temp;  
  always @(*) begin  
    out0 <= in0;  
    out1 <= in1;  
    if (swap) begin  
      temp <= out0;  
      out0 <= out1;  
      out1 <= temp;  
    end  
  end  
endmodule
```


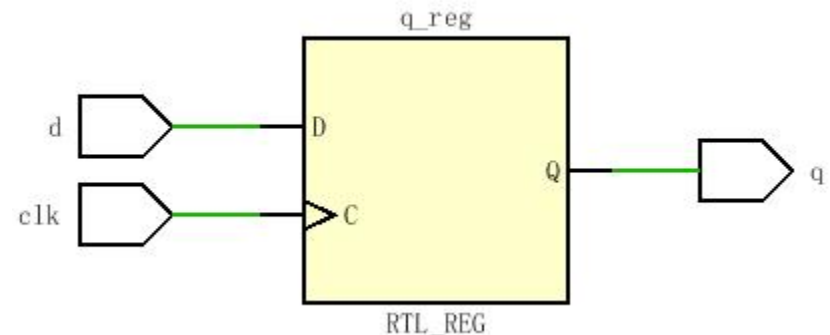
# More on Blocking

- Called blocking because....
  - ⑩ The evaluation of subsequent statements <RHS> are **blocked**, until the <LHS> assignment of the current statement is completed.

```
module pipe(clk, d, q);  
input clk,d;  
output q;  
reg q,q1,q2;  
always @(posedge clk) begin  
    q1 = d;  
    q2 = q1;  
    q  = q2;  
end //在一个时钟沿，d传递到q  
endmodule
```



# More on Non-Blocking

- With non-blocking statements the <RHS> of subsequent statements are not blocked. They are all evaluated simultaneously.

```
module pipe(clk, d, q);
```

```
input clk,d;
```

```
output q;
```

```
reg q,q1,q2;
```

```
always @(posedge clk) begin
```


```
    q1 <= d;
```

```
    q2 <= q1;
```

```
    q <= q2;
```

```
end //d传递到q需要间隔三个时钟
```

```
endmodule;
```

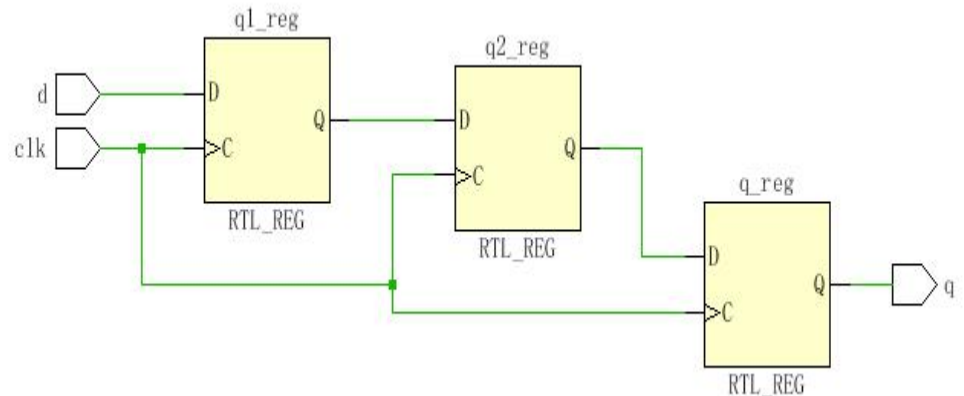

# So Blocking is no good and we should always use Non-Blocking??

---

- Consider combinational logic

```
module ao4(z,a,b,c,d);  
input a,b,c,d;  
output z;  
reg z,tmp1,tmp2;  
always @(a,b,c,d) begin  
    tmp1 <= a & b;  
    tmp2 <= c & d;  
    z <= tmp1 | tmp2;  
end  
endmodule
```

Does this work?

The inputs (a,b,c,d) in the sensitivity list change, and the always block is evaluated.

New assignments are scheduled for tmp1 & tmp2 variables.

A new assignment is scheduled for z using the **previous** tmp1 & tmp2 values.

# Why not non-Blocking for Combinational

- Can we make this example work?

```
module ao4(z,a,b,c,d);  
input a,b,c,d;  
output z;  
reg z,tmp1,tmp2;  
always @(a,b,c,d) begin  
    tmp1 <= a & b;  
    tmp2 <= c & d;  
    z <= tmp1 | tmp2;  
end  
endmodule
```

Yes

Put tmp1  
& tmp2 in  
the  
trigger  
list

```
module ao4(z,a,b,c,d);  
input a,b,c,d;  
output z;  
reg z,tmp1,tmp2;  
always @(a,b,c,d,tmp1,tmp2) begin  
    tmp1 <= a & b;  
    tmp2 <= c & d;  
    z <= tmp1 | tmp2;  
end  
endmodule
```

What is the downside of this?

# 任务(task)和 函数(function)

```
module Name (port list) ;
```

```
.....
```

```
task 任务名;  
    参数与类型说明;  
    局部变量说明; //静态的  
    过程语句  
endtask
```

```
function <位宽说明> 函数名;  
    输入参数与类型说明;  
    局部变量说明; //静态的  
    过程语句  
endfunction
```

```
endmodule
```

可以在模块不同位置执行共同代码

# 任务(task)和 函数(function)

## ❑ 差异

- 任务可以含有**时序控制**，而函数则没有；
- 任务可以有**输入和输出参数**，而**函数至少一个输入参数**，没有输出参数；
- **任务的调用是通过调用语句**，而**函数调用出现在表达式中**。



# functions

---

- 函数的定义和调用都包括在一个module内
  - 函数调用在表达式中 (RHS)
- 用于实现组合逻辑
  - 不能包含任何时延、时序、事件控制
  - 可以调用其他函数，不能调用任务
  - 只使用阻塞赋值，行为语句
- 输入/输出
  - 至少一个输入参数，不能有输出或者双向(inout)参数
  - 返回一个值，与函数同名的寄存器变量在函数中被隐式地声明，通过对该寄存器赋值来返回函数值，可以指定返回值的宽度 (缺省1-bit)

# Function Example

```
module arithmetic_unit (result_1, result_2, operand_1, operand_2,);
```

```
  output      [4: 0] result_1;
```

```
  output      [3: 0] result_2;
```

```
  input       [3: 0] operand_1, operand_2;
```

```
  assign result_1 = sum_of_operands (operand_1, operand_2);
```

```
  assign result_2 = larger_operand (operand_1, operand_2);
```

*function call*



```
function [4: 0] sum_of_operands(input [3:0] operand_1, operand_2);
```

```
  sum_of_operands = operand_1 + operand_2;
```

```
endfunction
```

*function output*



*function inputs*




```
function [3: 0] larger_operand(input [3:0] operand_1, operand_2);
```

```
  larger_operand = (operand_1 >= operand_2) ? operand_1 : operand_2;
```

```
endfunction
```

```
endmodule
```

# Function Example

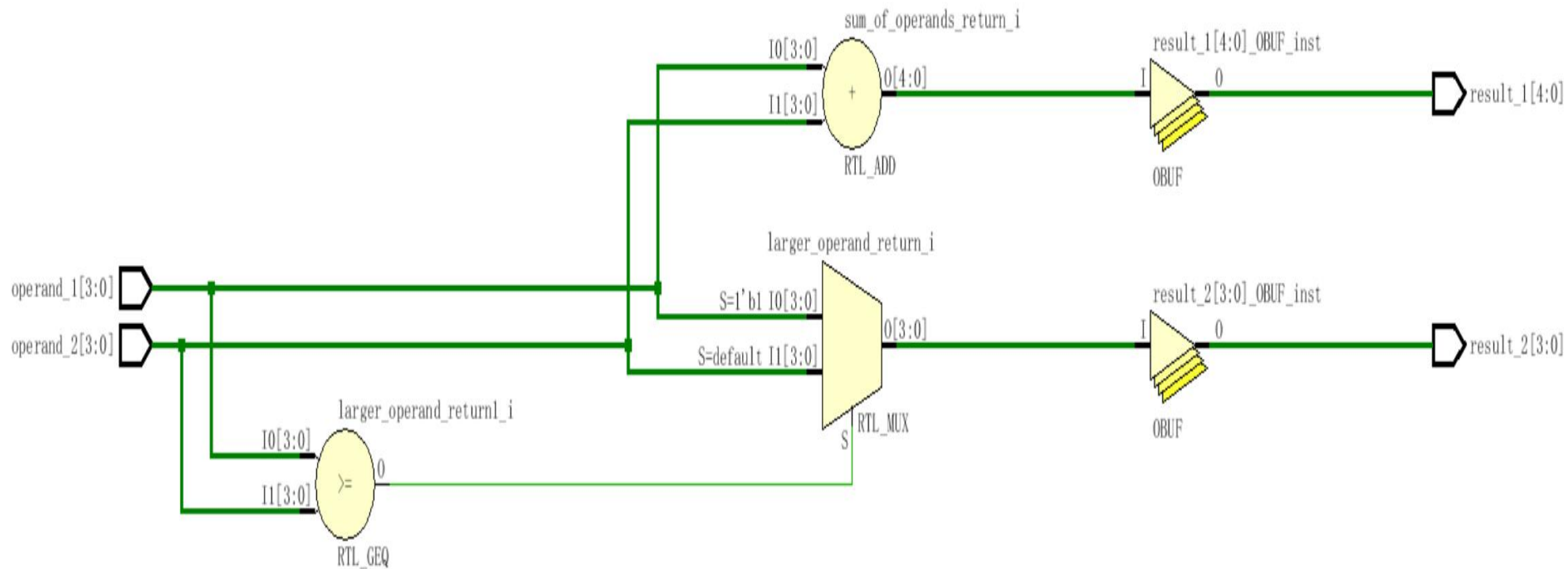

# tasks (much more useful than functions)

Functions	Tasks
函数只能调用其他函数，不能调用任务	任务可以调用其他任务和函数
函数不能包含任何延迟，事件或者时序控制	任务可以包含延迟，事件或者时序控制 (i.e. $\rightarrow$ @, #)
函数至少要有有一个输入参数，也可以有多个输入参数	任务可以没有或者有多个输入，输出，双向参数
函数只能返回一个值，不能有输出或者双向参数	任务不返回任何值，但是返回多个输出或双向参数值

# Why use Tasks?

---

- 把大程序分成小程序
- 在测试台上使用任务非常方便
  - 将常见的测试例程分解为任务
    - ✓ 初始化任务
    - ✓ 激励信号产生任务
    - ✓ 自检任务
  - 顶层测试主要是对任务的调用

# Task Example [Part 1]

```
module adder_task (c_out, sum,  
  output reg    [3: 0]  sum;  
  output reg    c_out;  
  input [3: 0]  data_a, data_b;  
  input        clk, reset, c_in;
```

## 任务调用:

- (1) 任务调用语句是过程性语句, 只能出现在**always** 语句或**initial** 语句中;
- (2) 任务调用语句中的参数列表顺序和类型必须和任务定义中的一致;
- (3) 输出参数必须是寄存器类型。

```
always @(posedge clk or posedge reset) begin
```

```
  if (reset) {c_out, sum} <= 0;
```

```
  else add_values (sum, c_out, data_a, data_b, c_in); //任务调用
```

```
end
```

```
// Continued on next slide
```

# Task Example

## 任务定义:

(1) 任务的参数不受限制

(2) 在任务中可以调用其他的任务或函数。

(3) 任务定义内不能出现 **initial** 和 **always** 过程块。

// Continued from previous

**task** add\_values;

**output reg** [3: 0] SUM;

**output reg** C\_OUT;

**input** [3: 0] DATA\_A, DATA\_B;

**input** C\_IN;

{C\_OUT, SUM} = DATA\_A + (DATA\_B + C\_IN);

**endtask**

**endmodule**


} **task outputs**

} **task inputs**

- Could have instead specified inputs/outputs using a port list.

**task** add\_values (**output reg** [3: 0] SUM, **output reg** C\_OUT,  
                  **input** [3:0] DATA\_A, DATA\_B, **input** C\_IN);

# Task Example [Part 3]

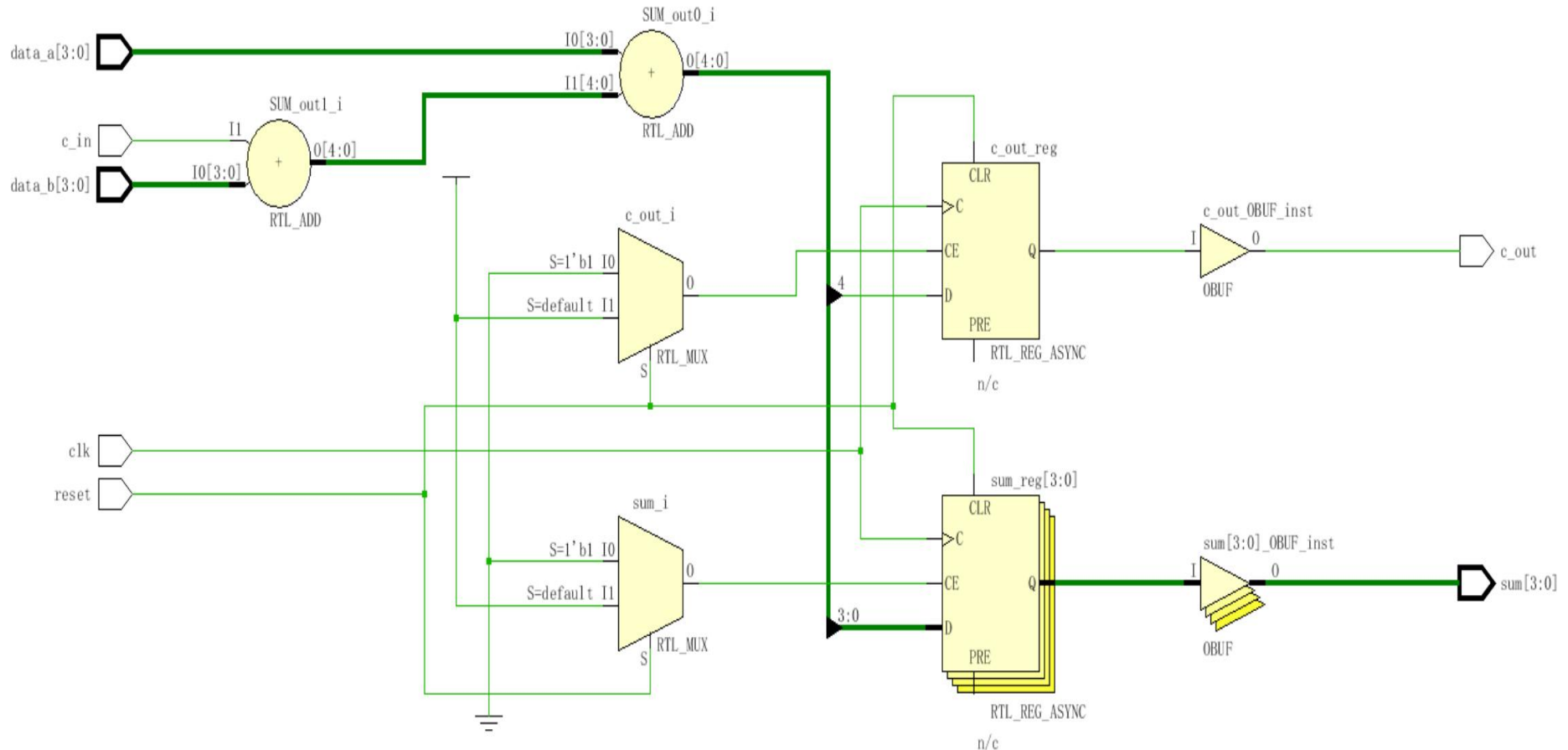



# 时序控制

- “#”符号引入的延迟控制，时间的长度由<time>值确定。

```
# <time> <statement> ;
```

- “@”符号引入的事件控制

```
@ (<posedge>|<negedge>|<signals> ) <statement>;
```

- 等待语句。表达式为真之前，延时下一个语句的执行。

```
wait (<expression>) <statement> ;
```

- 延迟定义块。对模块中某一指定的路径进行延迟定义，这一路径连接模块的输入端口与输出端口（或双向端口）。

```
specify
```

```
    (<expression>) = <time>;
```

```
    .....
```

```
endspecify
```

```
(a=>out)=9;
```

```
//从输入a到out的每位延迟为9
```


# 命名程序块

- Blocks (begin/end) or (fork/join) can be named
  - 命名块中可以声明局部变量;
  - 命名块中声明的变量可以通过层次名引用进行访问;
  - 命名块可以被禁用 (例如停止其执行)

```
module top();  
    initial begin: block1 //名字为block1的过程命名块  
        integer i;        // i 是block1命名块的静态局部变量  
        ...               //可以用层次名top.block1.i 被其他模块访问  
    end                   // end of block1  
endmodule
```
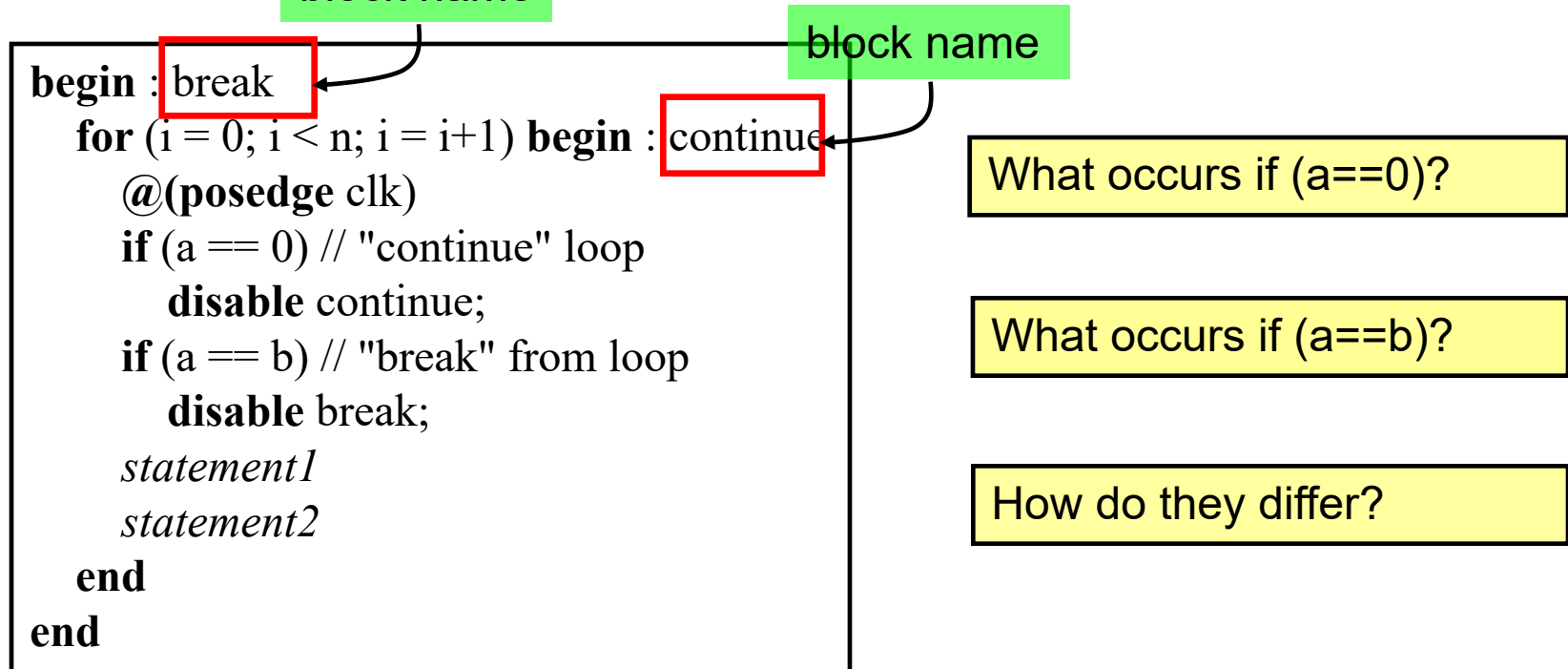
# disable Statement

- Similar to the “break” statement in C
  - Disables execution of the current block (not permanently)



# File I/O

- If we don't want to hard-code all information in the testbench, we can use input files
- Help automate testing
  - One file with inputs
  - One file with expected outputs
- Can have a software program generate data
  - Create the inputs for testing
  - Create “correct” output values for testing
  - Can use files to “connect” hardware/software system

# Opening/Closing Files

- **\$fopen** opens a file and returns an integer descriptor
  - integer fd = \$fopen(“filename”);**
  - integer fd = \$fopen(“filename”, r);**
  - If file cannot be open, returns a 0
  - Can output to more than one file simultaneously by writing to the OR ( | ) of the relevant file descriptors
    - ✓ Easier to have “summary” and “detailed” results
- **\$fclose** closes the file
  - \$fclose(fd);**

# Writing To Files

- Output statements have file equivalents
  - ✓ **\$fmonitor()**
  - ✓ **\$fdisplay()**
  - ✓ **\$fstrobe()**
  - ✓ **\$fwrite()**      // write is like a display without the \n
- These system calls take the file descriptor as the first argument
  - ✓ **\$fdisplay(fd, “out=%b in=%b”, out, in);**

# Reading From Files

- Read a binary file: **\$fread**(destination, fd);
  - Can specify start address & number of locations too
  - Good luck! I have never used this.
- Very rich file manipulation (see IEEE Standard)
  - ✓ \$fseek(), \$fflush(), \$ftell(), \$rewind(), ...
- Will cover a few of the more common read commands next

# Using **\$fgetc** to read characters

```
module file_read()
parameter EOF = -1;
integer file_handle,error,indx;
reg signed [15:0] wide_char;
reg [7:0] mem[0:255];
reg [639:0] err_str;

initial begin
    indx=0;
    file_handle = $fopen("text.txt","r");
    error = $ferror(file_handle,err_str);
    if (error==0) begin
        wide_char = 16'h0000;
        while (wide_char!=EOF) begin
            wide_char = $fgetc(file_handle);
            mem[indx] = wide_char[7:0];
            $write("%c",mem[indx]);
```

```
            indx = indx + 1;
        end
    end
    else $display("Can't open file...");
    $fclose(file_handle);
end
endmodule
```

The quick brown fox jumped  
over the lazy dogs

*text.txt*

When finished the array *mem* will contain the characters of this file one by one, and the file will have been echoed to the screen.

Why wide\_char[15:0] and why signed?



# Using **\$fgets** to read lines

```
module file_read2()

integer file_handle,error,indx,num_bytes_in_line;
reg [256*8:1] mem[0:255],line_buffer;
reg [639:0] err_str;

initial begin
    indx=0;
    file_handle = $fopen("text2.txt","r");
    error = $ferror(file_handle,err_str);
    if (error==0) begin
        num_bytes_in_line = $fgets(line_buffer,file_handle);
        while (num_bytes_in_line>0) begin
            mem[indx] = line_buffer;
            $write("%s",mem[indx]);
            indx = indx + 1;
            num_bytes_in_line = $fgets(line_buffer,file_handle);
        end
    end
    else $display("Could not open file text2.txt");
```

**\$fgets()** returns the number of bytes in the line. When this is a zero you know you hit EOF.

# Using **\$fscanf** to read files

```
module file_read3()
integer file_handle,error,indx,num_matches;
reg [15:0] mem[0:255][1:0];
reg [639:0] err_str;

initial begin
    indx=0;
    file_handle = $fopen("text3.txt","r");
    error = $ferror(file_handle,err_str);
    if (error==0) begin
        num_matches = $fscanf(file_handle,"%h %h",mem[indx][0],mem[indx][1]);
        while (num_matches>0) begin
            $display("data is: %h %h",mem[indx][0],mem[indx][1]);
            indx = indx + 1;
            num_matches = $fscanf(file_handle,"%h %h",mem[indx][0],mem[indx][1]);
        end
    end
    else $display("Could not open file text3.txt");
```

12f3	13f3
abcd	1234
3214	21ab

<i>text3.txt</i>
------------------

# Loading Memory Data From Files

- This is very useful (memory modeling & testbenches)
  - **\$readmemb**("<file\_name>",<memory>);
  - **\$readmemb**("<file\_name>",<memory>,<start\_addr>,<finish\_addr>);
  - **\$readmemh**("<file\_name>",<memory>);
  - **\$readmemh**("<file\_name>",<memory>,<start\_addr>,<finish\_addr>);
- **\$readmemh** → Hex data...**\$readmemb** → binary data
  - But they are reading ASCII files either way (just how numbers are represented)

// addr    data
@0000 10100010
@0001 10111001
@0002 00100011

example "binary"  
file

// addr    data
@0000    A2
@0001    B9
@0002    23

example "hex"  
file

//data
A2
B9
23

address is optional  
for the lazy

# Example of \$readmemh

```
module rom(input clk; input [7:0] addr; output [15:0] dout);
```

```
reg [15:0] mem[0:255];    // 16-bit wide 256 entry ROM
```

```
reg [15:0] dout;
```

```
initial
```

```
    $readmemh("constants",mem);
```

```
always @(negedge clk) begin
```

```
    //////////////////////////////////////////////////////////////////
```


```
    // ROM presents data on clock low //
```

```
    //////////////////////////////////////////////////////////////////
```

```
    dout <= mem[addr];
```

```
end
```

```
endmodule
```

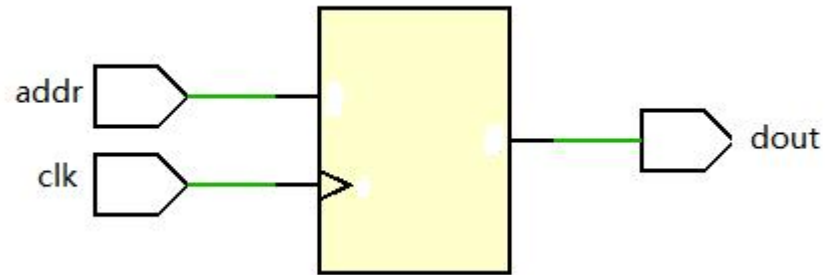

# 'Include Compiler Directives

- **`include** filename

- Inserts entire contents of another file at compilation
- Can be placed anywhere in Verilog source
- Can provide either relative or absolute path names

- Example 1:

```
module use_adder8(...);
```

```
  `include "adder8.v" // include the task for adder8
```

- Example 2:

```
module cppc_dig_tb();
```

```
  `include "/home/ehoffman/ece551/project/tb_tasks.v"
```

- Useful for including tasks and functions in multiple modules